 


ECE 154A Lab 4**a. Hours spent on lab:** Roughly 10**b. Table 1: First sixteen cycles of test code from textbook Fig. 7.60**


Cycle	reset	pc	Instr	branch	srca	srcb	alurest	zero	pcsrc	Writedata	mem write	read data
1	1	00	addi \$2, \$0, 5 20020005	0	0	5	5	0	0	0 X	0	X
2	0	04	addi \$3, \$0, 12 2003000C	0	0	C	C	0	0	0 X	0	X
3	0	08	addi \$7, \$3, -9 20067FFF7	0	C	-9	3	0	0	0 X	0	X
4	0	0C	or \$4, \$7, \$2 00E22025	0	3	5	7	0	0	5	0	X
5	0	10	and \$5, \$3, \$4 00642824	0	12	7	4	0	0	7	0	X
6	0	14	add \$5, \$5, \$4 00A42820	0	4	7	11	0	0	7	0	X
7	0	18	beq \$5, \$7, end 10A7000A	1	11	3	8	0	0	3	0	X
8	0	1C	slt \$4, \$3, \$4 0064202A	0	12	7	0	1	0	7	0	X
9	0	20	beq \$4, \$0, around 10800001	1	0	0	0	1	1	0	0	X
10	0	28	slt \$4, \$7, \$2 00E2202A	0	3	5	1	0	0	5	0	X
11	0	2C	add \$7, \$4, \$4 00853820	0	1	11	12	0	0	11	0	X
12	0	30	sub \$7, \$7, \$2 00E23822	0	12	5	7	0	0	5	0	X
13	0	34	sw \$7, 68(\$3) ac670044	0	12	68	80	0	0	7	1	X
14	0	38	lw \$2, 80(\$0) 8C020050	0	0	80	80	0	0	X	0	7
15	0	3C	j end 08000011	0	X	X	XX	X	0	X	0	X
16	0	44	sw \$2, 84(\$0) AC020054	0	0	84	84	0	0	7	1	X

The sw instruction at PC = 0x44 of the program in memfile.dat **writes 0x0000 0007 (7) to memory address 0x54 (84)**


c. Simulation waveforms of original processor:
0-160ns (setup time + first 8 cycles)



160-320ns (second 8 cycles)

 

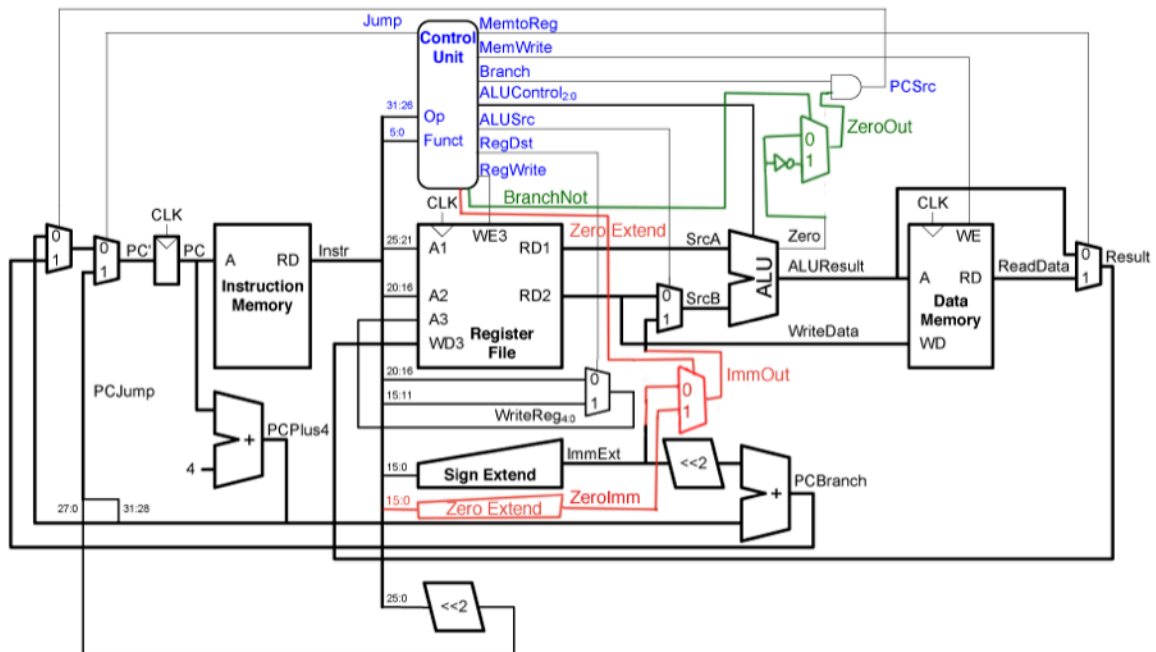d. Modifications to support ori and bne operations
Modified datapath:



Modified Single-cycle MIPS processor

A new signal, BranchNot, should be added such that the input to the AND gate for PCSrc is selected by a 2:1 multiplexer - an input of 0 propagates the unchanged Zero signal from the ALU, used for the beq operation, while an input of 1 instead connects the Zero signal through a NOT gate, to be used for the bne operation.

A new signal, ZeroExtend, should be added such that the input to port 1 of the SrcB multiplexer to the ALU is selected by a 2:1 multiplexer - an input of 0 propagates ImmExt, the sign-extended immediate, used for existing operations, while an input of 1 instead connects a zero-extended version of the immediate, used for the ori operation.

See section F for modified main decoder table, Table 2

Modified ALU decoder table:

ALUOp _{1:0}	Meaning	Funct _{5:0}	Meaning	ALUControl _{2:0}
00	Add	X	Add	010
01	Subtract	X	Subtract	110
10	Look at funct field	100000	Add (R-type)	010
		100010	Subtract (R-type)	110
		100100	AND (R-type)	000
		100101	OR (R-type)	001
		101010	SLT (R-type)	111
11	Or	X	OR (I-type)	001

For the bne operation, all existing control signals are the same as those of the beq operation. The new signal, BranchNot, is 1 for bne, and 0 for all other operations.

To support the ori operation, the main decoder should output 11 for APUOp_{1:0}, and the ALU decoder should output 001 in response to this signal. The new signal, ZeroExtend, should be 1 for ori and 0 for all other existing operations. All other control signals for ori should be the same as those of the addi operation.

e. Verilog code for the modified MIPS processor

Testbench.v

```
// Testbench for MIPS processor
// Issues reset signal then cycles clock repeatedly
module tb;
    reg clk;
    reg reset;
    top topModule(clk, reset); // Instantiate MIPS top module
    reg i;

    initial begin
        clk = 0;
        reset = 0;
        #10;
        reset = 1;
        clk = 1;
        #10
        reset = 0;
        clk = 0;
        for (i = 0; i < 16; i = i + 1) begin
            // Cycle clock
            #10
            clk = 1;
            #10
            clk = 0;
        end
    end
end

endmodule
```

mipstop.v:

```
// Top level system including MIPS and memories
// Unmodified from provided code

module top(input clk, reset);

    wire [31:0] pc, instr, readdata;
    wire [31:0] writedata, dataadr;
    wire        memwrite;

    // processor and memories are instantiated here
    mips mips(clk, reset, pc, instr, memwrite, dataadr, writedata,
readdata);
    imem imem(pc[7:2], instr);
    dmem dmem(clk, memwrite, dataadr, writedata, readdata);

endmodule
```

mipsmem.v:

// External memories used by MIPS single-cycle processor

// Data memory implementation

```
module dmem(input      clk, we,
            input  [31:0] a, wd,
            output [31:0] rd);
```

```
// 64 bit storage of 32-bit words
reg [31:0] RAM[63:0];
```

```
// Always read
assign rd = RAM[a[31:2]];
```

```
always @(posedge clk) begin
    // Write if enabled
    if (we) begin
        RAM[a[31:2]] <= wd;
    end
end
```

```
endmodule
```

// Instruction memory (already implemented)

```
module imem(input  [5:0] a,
            output [31:0] rd);
```

```
    reg [31:0] RAM[63:0];
```

```
    initial
    begin
        $readmemh("memfile2.dat",RAM); // Initialize memory with program
    end
```

```
    assign rd = RAM[a]; // word aligned
endmodule
```

mips.v:

// Single-cycle MIPS processor

// Instantiates a controller and a datapath module

```
module mips(input          clk, reset,
            output [31:0] pc,
            input  [31:0] instr,
            output          memwrite,
            output [31:0] aluout, writedata,
            input  [31:0] readdata);

    wire      memtoreg, branch,
              pcsrc, zero,
              alusrc, regdst, regwrite, jump;
    wire [2:0] alucontrol;

    // ADDED: wire for zeroExtend signal
    wire zeroExtend;

    // ADDED: zeroExtend output from controller, input to datapath
    controller c(instr[31:26], instr[5:0], zero,
                 memtoreg, memwrite, pcsrc,
                 alusrc, regdst, regwrite, jump,
                 alucontrol, zeroExtend);
    datapath dp(clk, reset, memtoreg, pcsrc,
                alusrc, regdst, regwrite, jump,
                alucontrol,
                zero, pc, instr,
                aluout, writedata, readdata, zeroExtend);
endmodule

// Controller module
module controller(input  [5:0] op, funct,
                  input      zero,
                  output      memtoreg, memwrite,
                  output      pcsrc, alusrc,
                  output      regdst, regwrite,
                  output      jump,
                  output [2:0] alucontrol,
                  output zeroExtend); // ADDED: ZeroExtend output to
datapath

    wire [1:0] aluop;
    wire branch;
    wire branchNot; // ADDED: branchNot signal for bne operation
```

```

// ADDED: zeroExtend output from main decoder
mainDecoder dec(op, memtoreg, memwrite, branch, alusrc, regdst,
regwrite, jump, aluop, branchNot, zeroExtend);
aluDecoder aluDec(funct, aluop, alucontrol);

// Modification for branchNot here
wire zeroOut;
wire zeroNot;
not zeroNotGate(zeroNot, zero);
mux2 #(1) branchMux(zero, zeroNot, branchNot, zeroOut);
assign pcsrc = branch & zeroOut; // Changed from branch & zero

endmodule

// Datapath
module datapath(input          clk, reset,
                input          memtoreg, pcsrc,
                input          alusrc, regdst,
                input          regwrite, jump,
                input  [2:0]    alucontrol,
                output         zero,
                output  [31:0] pc,
                input  [31:0] instr,
                output  [31:0] aluout, writedata,
                input  [31:0] readdata,
                input zeroExtend); // ADDED: zeroExtend input from
controller

wire [4:0] writereg;
wire [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
wire [31:0] signimm, signimmsh;
wire [31:0] srca, srcb;
wire [31:0] result;

// Determine next PC
reset_ff #(32) pcreg(clk, reset, pcnext, pc);
adder pcadd1(pc, 32'b100, pcplus4);
sl2 immsh(signimm, signimmsh);
adder pcadd2(pcplus4, signimmsh, pcbranch);
mux2 #(32) pcbrmuc(pcplus4, pcbranch, pcsrc, pcnextbr);
wire [31:0] pcmuxd0;
assign pcmuxd0[31:0] = {pcplus4[31:28], instr[25:0], 2'b00};
mux2 #(32) pcmux(pcnextbr, pcmuxd0, jump, pcnext);

// Register file
regfile rf(clk, regwrite, instr[25:21], instr[20:16], writereg,
result, srca, writedata);
mux2 #(5) wrmux(instr[20:16], instr[15:11], regdst, writereg);
mux2 #(32) resmux(aluout, readdata, memtoreg, result);

```



```

signext se(instr[15:0], signimm);

// ADDED: logic for zeroExtend
wire [31:0] zeroImm;
zeroext zext(instr[15:0], zeroImm);
wire [31:0] immOut;
mux2 #(32) immMux(signimm, zeroImm, zeroExtend, immOut);

// ALU
// ADDED: changed signimm to immOut to get signal from mux
mux2 #(32) srcbmux(writedata, immOut, alusrc, srcb);
alu alu(srca, srcb, alucontrol, aluout, zero);

endmodule

```


controller.v:

```
module mainDecoder(    input [5:0] op,
                      output reg memtoreg,
                      output reg memwrite,
                      output reg branch,
                      output reg alusrc,
                      output reg regdst,
                      output reg regwrite,
                      output reg jump,
                      output reg [1:0] aluop,
                      output reg branchNot,
                      output reg zeroExtend);

// Main decoder
reg [10:0] controls; // ADDED two bits for branchNot and zeroExtend

always @ (*) begin
    case(op)
        // Controls register modified to include branchNot,
        // zeroExtend signals
        6'b000000: controls <= 11'b001100000010; // R-type
        6'b100011: controls <= 11'b00101001000; // lw
        6'b101011: controls <= 11'b00001010000; // sw
        6'b000100: controls <= 11'b000000100001; // beq
        6'b001000: controls <= 11'b00101000000; // addi
        6'b000010: controls <= 11'b000000000100; // j
        6'b001101: controls <= 11'b101010000011; // ADDED: ori
        6'b000101: controls <= 11'b010001000001; // ADDED: bne
        default: controls <= 11'bxxxxxxxxxx; // invalid opcode
    endcase
    zeroExtend = controls[10]; // ADDED: zeroExtend
    branchNot = controls[9]; // ADDED: branchNot
    regwrite = controls[8];
    regdst = controls[7];
    alusrc = controls[6];
    branch = controls[5];
    memwrite = controls[4];
    memtoreg = controls[3];
    jump = controls[2];
    aluop = controls[1:0];
end
endmodule

module aluDecoder(    input [5:0] funct,
                     input [1:0] aluop,
                     output reg [2:0] alucontrol);

// ALU decoder
always @ (*) begin
    case (aluop)
```

```

2'b00: alucontrol <= 3'b010; // add for lw, sw, addi
2'b01: alucontrol <= 3'b110; // sub for beq
2'b11: alucontrol <= 3'b001; // ADDED: or for ori operation
default: case (funct)          // R-type functions
    6'b100000: alucontrol <= 3'b010; // add
    6'b100010: alucontrol <= 3'b110; // sub
    6'b100100: alucontrol <= 3'b000; // and
    6'b100101: alucontrol <= 3'b001; // or
    6'b101010: alucontrol <= 3'b111; // slt
    default: alucontrol <= 3'bxxx; // invalid data in
func field
    endcase
endcase
end
endmodule

```

```

datapath.v:
// Datapath modules

// Register file
module regfile( input reg clk,
                input reg we3,
                input reg [4:0] ra1, ra2, wa3,
                input reg [31:0] wd3,
                output [31:0] rd1, rd2);
reg [31:0] rf [31:0];

always @ (posedge clk) begin
    if (we3) begin
        rf[wa3] <= wd3;
    end
end

assign rd1 = (ra1 != 0) ? rf[ra1] : 0;
assign rd2 = (ra2 != 0) ? rf[ra2] : 0;
endmodule

// Adder
module adder(    input reg [31:0] a, b,
                output [31:0] y);
assign y = a + b;
endmodule

// Bitshift left by 2
module sl2(      input reg [31:0] a,
                output [31:0] y);
assign y = {a[29:0], 2'b00};
endmodule

// Sign extension
module signext( input reg [15:0] a,
                output [31:0] y);
assign y = {{16{a[15]}}, a};
endmodule

// Variable-width resettable flip-flop
module reset_ff #(parameter WIDTH = 8)(
    input reg clk, reset,
    input reg [(WIDTH-1):0] d,
    output reg [(WIDTH-1):0] q);
always @ (posedge clk, posedge reset)
    if (reset) begin
        q <= 0;
    end
    else begin

```

```
        q <= d;
    end
endmodule
```

```
// Variable-width 2:1 multiplexer
module mux2 #(parameter WIDTH = 8)(
    input reg [(WIDTH-1):0] d0,
    input reg [(WIDTH-1):0] d1,
    input reg s,
    output [(WIDTH-1):0] y);
assign y = s ? d1 : d0;
endmodule
```

```
// ADDED: zero extension module for ori operation
module zeroext( input reg [15:0] a,
    output [31:0] y);
assign y = {16'b0000000000000000, a};
endmodule
```

alu.v:

```
// ALU from Lab 1 - unmodified
module alu(input [31:0] a, b, input [2:0] f, output [31:0] y, output
zero);
```

```
reg [31:0] addB; // signal fed to full adder
wire [31:0] addY; // number from full adder
wire [31:0] aandb; // A & (~)B
wire [31:0] aorb; // A | (~)B
wire [31:0] asltb; // A SLT B
```

```
fullAdder FA(a, addB, f[2], addY);
```

```
// Bitwise operations
assign aandb = (a & addB);
assign aorb = (a | addB);
```

```
// SLT from sign bit of adder result, zero extend
assign asltb[31:1] = 31'b00000000000000000000000000000000;
assign asltb[0] = (addY[31] == 1);
```

```
// Buffer for output
reg[31:0] y_out;
assign y = y_out;
```

```
// Maps B/~B as appropriate, output to correct function result
always @ * begin
```

```
case(f[2])
    0: addB = b;
    1: addB = ~b;
    default: addB = 32'h00000000;
endcase
case(f)
    0: y_out = aandb;
    1: y_out = aorb;
    2: y_out = addY;
    4: y_out = aandb;
    5: y_out = aorb;
    6: y_out = addY;
    7: y_out = asltb;
    default: y_out = 32'h00000000;
endcase
```

```
end
assign zero = (y == 32'h00000000); // If output is zero, toggle zero
endmodule
```

```
module fullAdder(input [31:0] a, b, input cin, output [31:0] y);
    assign y = a + b + cin;
endmodule
```

f. Tables 2 and 3 for the modified MIPS processor:

Table 2: Extended functionality for the main decoder

Instruction	Op _{5:0}	Reg Write	RegDst	AluSrc	Branch	MemWrite	Memto Reg	ALU Op _{1:0}	Jump	Branch Not	ZeroExtend
R-type	000000	1	1	0	0	0	0	10	0	0	0
lw	100011	1	0	1	0	0	1	00	0	0	0
sw	101011	0	X	1	0	1	X	00	0	0	0
beq	000100	0	X	0	1	0	X	01	0	0	0
addi	001000	1	0	1	0	0	0	00	0	0	0
j	000010	0	X	X	X	0	X	XX	1	0	0
ori	001101	1	0	1	0	0	0	11	0	0	1
bne	000101	0	X	0	1	0	X	01	0	1	0

Table 3: Extended functionality for the ALU decoder

ALUOp _{1:0}	Meaning
00	Add
01	Subtract
10	Look at funct field
11	OR

g. Contents of memfile2.dat, machine code translation of test2.asm:


```

34088000
20098000
350A8001
11280005
0128582A
15600001
08000005
01485022
350800FF
016A5820
01484022
AD680052


```

h. Simulation waveforms of modified processor

0-150ns (setup time + first 7 cycles)

 

150-300ns (last 4 cycles)

 

The sw instruction at PC 0x30 of test2.asm writes 0xFFFF 7F02 (-33022) to memory address 0x54 (84)

Addendum: Translation of test2.asm into machine code

main: (PC = 0x00)

ori \$t0 \$0, 0x8000

op	rs (source)	rt (source/destination)	imm
13	0	8	0x8000
0011 01	00 000	0 1000	1000 0000 0000 0000

0x34088000

addi \$t1, \$0, -32768

op	rs (source)	rt (source/destination)	imm
8	0	9	-32768
0010 00	00 000	0 1001	1000 0000 0000 0000

0x20098000

ori \$t2, \$t0, 0x8001

op	rs (source)	rt (source/destination)	imm
13	8	10	0x8001
0011 01	01 000	0 1010	1000 0000 0000 0001

0x350A8001

beq \$t0, \$t1, there (PC = 0x0C)

op	rs (source)	rt (source/destination)	imm
4	9	8	BTA = 0x24 SignImm = 0x24 - 0x10 = 0x14 >> 2 = 5
0001 00	01 001	0 1000	0000 0000 0000 0101

0x11280005

slt \$t3, \$t1, \$t0

op	rs (source)	rt (source)	rd (destination)	shamt	funct
0	9	8	11	0	42
0000 00	01 001	0 1000	0101 1	000 00	10 1010

0x0128582A

bne \$t3, \$0, here (PC = 0x14)

op	rs (source)	rt (source/destination)	imm
5	11	0	BTA = 0x1C SignImm = 0x1C - 4 - 0x14 = 0x08 >> 2 = 1
0001 01	01 011	0 0000	0000 0000 0000 0001

0x15600001

j there (PC = 0x18)

op	address
2	JTA = 0x24 0000 0000 0010 0100
0000 10	00 0000 0000 0000 0000 0000 0101

0x08000005

here: (PC = 0x1C)

sub \$t2, \$t2, \$t0

op	rs (source)	rt (source)	rd (destination)	shamt	funct
0	10	8	10	0	34
0000 00	01 010	0 1000	0101 0	000 00	10 0010

0x01485022

ori \$t0, \$t0, 0xFF

op	rs (source)	rt (source/destination)	imm
13	8	8	0xFF
0011 01	01 000	0 1000	0000 0000 1111 1111

0x350800FF

there: (PC = 0x24)

add \$t3, \$t3, \$t2

op	rs (source)	rt (source)	rd (destination)	shamt	funct
0	11	10	11	0	32
0000 00	01 011	0 1010	0101 1	000 00	10 0000

0x016A5820

sub \$t0, \$t2, \$t0

op	rs (source)	rt (source)	rd (destination)	shamt	funct
0	10	8	8	0	34
0000 00	01 010	0 1000	0100 0	000 00	10 0010

0x01484022

sw \$t0, 82(\$t3)

op	rs (source)	rt (source/destination)	imm
43	11	8	82
1010 11	01 011	0 1000	0000 0000 0101 0010

0xAD680052

Ideal Program operation:

PC	Instruction performed
0x00	\$t0 = 0x0000 8000
0x04	\$t1 = 0xffff 8000
0x08	\$t2 = 0x0000 8001
0x0C	branch if \$t0 and \$t1 are equal - they're not
0x10	\$t3 = #t1 < \$t0 = 1
0x14	branch if \$t3 ≠ 0, yes, go to 'here' => PC = 0x1C
0x18	Not executed
0x1C	\$t2 = 0x0000 0001
0x20	\$t0 = 0x0000 80FF (33023)
0x24	\$t3 = \$t3 + \$t2 = 1 + 1 = 2
0x28	\$t0 = \$t2 - \$t0 => 1 - 33023 => -33022 => 0xFFFF7F02
0x2C	\$t0 saved to \$t3 + 82 => -33022 stored in 84